

CSC3050 Tutorial

Introduction to Verilog

Teaching Assistants

- Wei Dai (戴维)
 - Email: weidai@link.cuhk.edu.cn
 - Office Hour:
 - We. 21:00 – 22: 00 or by appointment
- Mickey MA (马毓琦)
 - Email: mickeyma@cuhk.edu.cn
 - Office Hour:
 - Tu. 21:00 – 22: 00 or by appointment
- - Tutorial Room
 - Time: Mo. Tu. We. 19:00 - 21:00 (Consulting sessions)
 - ZOOM ID: 962 2765 8133
 - Password: CSC3050

Overview of Verilog


- **Objectives**
- **Verilog Basics**
 - **Notation**
 - **Keywords & Constructs**
 - **Operators**
- **Types of Descriptions**
 - **Structural**
 - **Dataflow**
 - **Behavioral & Hierarchical**

Objectives


- **To become familiar with the hardware description language (HDL) approach to specifying designs**
 - **Be able to read a simple Verilog HDL description**
 - **Be able to write a simple Verilog HDL description using a limited set of syntax and semantics**
 - **Understanding the need for a “hardware view” when reading and writing an HDL**

What is HDL?

Describe a Module

 

Test a Module

 

Verilog Notation - 1

- **Verilog is:**
 - **Case sensitive**
 - **Based on the programming language C**
- **Comments**
 - **Single Line**
`//` [end of line]
 - **Multiple Line**
`/*`

`*/`
- **List element separator:** `,`
- **Statement terminator:** `;`

Verilog Notation - 2

- **Binary Values for Constants and Variables**
 - **0**
 - **1**
 - **X,x** - Unknown
 - **Z,z** – High impedance state (open circuit)
- **Constants**
 - **n'b[integer]:** 1'b1 = 1, 8'b1 = 00000001, 4'b0101= 0101, 8'bxxxxxxxx, 8'bxxxx = 0000xxxx
 - **n'h[integer]:** 8'hA9 = 10101001, 16'hf1= 0000000011110001
- **Identifier Examples**
 - **Scalar:** A,C,RUN,stop,m,n
 - **Vector:** sel[0:2], f[0:5], ACC[31:0], SUM[15:0], sum[15:0]

Verilog Keywords & Constructs - 1

- Keywords are lower case
- **module** – fundamental building block for Verilog designs
 - Used to construct design hierarchy
 - Cannot be nested
- **endmodule** – ends a module – not a statement
=> no “;”
- Module Declaration
 - **module** *module_name* (*module_port*, *module_port*, ...);
 - Example: **module** full_adder (A, B, c_in, c_out, S);

Verilog Keywords & Constructs - 2

- **Input Declaration**
 - **Scalar**
 - **input** *list of input identifiers*;
 - Example: input A, B, c_in;
 - **Vector**
 - **input**[*range*] *list of input identifiers*;
 - Example: input[15:0] A, B, data;
- **Output Declaration**
 - **Scalar Example:** **output** c_out, OV, MINUS;
 - **Vector Example:** **output**[7:0] ACC, REG_IN, data_out;

Verilog Keywords & Constructs - 3

- **Two Major Data Type**
 - wire: wire in a chip.
 - reg: register for storing data.
- **Primitive Gates**
 - **not, and, or, nand, nor, xor, xnor**
 - Syntax: *gate_operator instance_identifier (output, input_1, input_2, ...)*
 - Examples:
 - and** A1 (F, A, B); //F = A B
 - or** O1 (w, a, b, c)
 - O2 (x, b, c, d, e); //w=a+b+c,x=b+c+d+e

Verilog Operators - 1

- Bitwise Operators

- ~ NOT

- & AND

- | OR

- ^ XOR

- ^~ or ~^ XNOR

- Example: **input**[3:0] A, B;
output[3:0] Z ;
assign Z = A | ~B;

Verilog Operators - 2

- **Arithmetic Operators**
+, -, (plus others)
- **Logical & Relational Operators**
!, &&, ||, ==, !=, >=, <=, >, < (plus others)
- **Concatenation & Replication Operators**
{identifier_1, identifier_2, ...}
{n{identifier}}
 - Examples: {REG_IN[6:0],Serial_in},
{8 {1'b0}}

Dataflow Verilog

- Circuit function can be described by assign statements using Boolean equations. (Concurrency)
- `assign [delay] LHS_net = RHS_expression:`

```
module fig519d (A0, B0, C0, C1, S0);  
    input A0, B0, C0;  
    output C1, S0;  
    wire [1:0] N;  
    assign N[1] = ~(A0 & B0);  
    assign N[0] = ~(A0 | B0);  
    assign C1 = ~((N[1] & ~C0) | N[0]);  
    assign S0 = (~N[0] & N[1]) ^ (~(~C0));  
endmodule
```

Behavioral Verilog - 1

- There is often a sequential process associated with event control in the always statement.

```
module FA_Seq (A, B, Cin, Sum, Cout) ;  
    input  A, B, Cin ;  
    output Sum, Cout;  
    reg Sum, Cout;  
    always @ (A or B or Cin)  
    begin  
        Sum = (A ^ B) ^ Cin  
        Cout = A & Cin;  
    end  
endmodule
```

Behavioral Verilog - 2

initial statement includes a sequential process, which will be executed at 0ns, and after completion, it will be suspended forever.

```
module Test;  
  initial  
    begin  
      Pop = 0  
      Pip = 0  
      #5 Pop = 1  
      #3 Pid = 1  
    end  
endmodule
```

Structural Verilog

- Circuits can be described by a netlist as a text alternative to a diagram - Example :

```
module decoder(A0, B0, C0, C1, S0);  
    input A0, B0, C0;  
    output C1, S0;  
    wire[1:7] N;  
    not G1 (N[3],C0), G2 (N[5],N[2]), G3 (N[6],N[3]);  
    nand G4 (N[1],A0,B0);  
    nor G5 (N[2],A0,B0), G6 (C1,N[2],N[4]);  
    and G7 (N[4],N[1],N[3]), G8 (N[7],N[1],N[5]);  
    xor G9 (S0,N[6],N[7]);  
endmodule
```


Hierarchical Verilog

```
module add (X, Y, C_in, S);  
    input [3:0] X, Y;  
    input C_in;  
    output [3:0] S;  
    assign S = X + Y + {3'b0, C_in};  
endmodule  
  
module M1comp (data_in, data_out, comp);  
    input[3:0] data_in;  
    input comp;  
    output [3:0] data_out;  
    assign data_out = {4{comp}} ^ data_in;  
endmodule
```

Key points about Module Structure

- If you use Verilog to implement some functions, you must first find out which ones need to be executed concurrently and which ones need to be executed sequentially.
- “Assign” statement, “always” block is executed concurrently. Their sequence will not affect the logics of the function.
- Inside “always” block, logic is executed sequentially.

Test Bench

- Test Bench is a test module used to verify whether the working state of the designed circuit is correct:
- Add activation to the input signal of the circuit, and verify whether the circuit works normally by observing the output signal.

Common Form:

```
module test;
    reg ...;
    wire ...;
    initial begin ...; ...; ...; end    //generate testing signal
    always #delay begin ...; end //generate testing signal
    // Instance reference of the module under test
    initial begin ...; ...; ...; end //record the output signal
endmodule
```