

CSC3050 Tutorial

Sequential Logic And Combinational Logic in Verilog

Outline

- Sequential logic and combinational logic in Verilog
 - **Combinational** Logic Circuit With “**Assign**” Statement;
 - **Combinational** Logic Circuit With “**Always**” Block;
 - **Sequential** Logic Circuit With “**Always**” Block;
- Blocking and Non-blocking Assignments
- Example of D flipflop.


Differences Between Combinational & Sequential Logic

- Combinational logic circuit
 - Output at any time only depends on the input.
 - It has nothing to do with the circuit state.
(Stateless)
- Sequential logic circuit
 - Output depends on both the input and the circuit state at current time.

Combinational Logic Circuit With “Assign” Statement

Take two-way selector as example:
 
```
module mux2to1(a, b, sel, out);  
    input  a, b;  
    input  sel;  
    output out;  
    assign out = (sel)? b : a;  
endmodule
```




Note:

Only wire type data can be assigned value in the “Assign” statement.

Combinational Logic Circuit With “Always” Block

Still take two-way selector as example:
 
```
module mux2to1(a, b, sel, out);  
    input  a, b;  
    input  sel;  
    output out;  
    reg out;  
    always @ (sel or a or b)  
        out = (sel) ? b : a;  
endmodule
```




Note:

- 1: Only reg type data can be assigned values in “Always” block.
- 2: Combinational logic circuit implemented by “Always” block is level triggered.

Combinational logic

The effect of combinational logic described by “always” block and “assign” statement is the same.

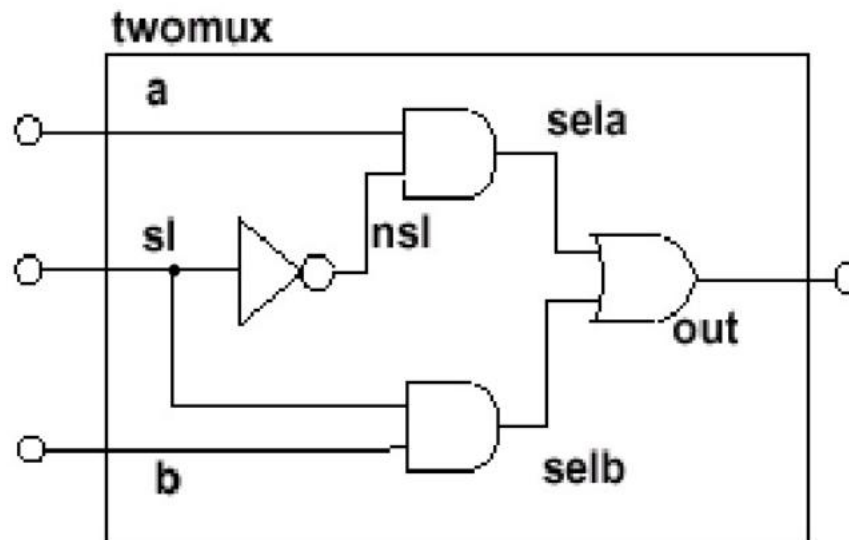The former 2 ways to define two-way selector will generate the same circuit as follows.



Sequential Logic Circuit With “Always” Block

```
module DFF(clk, rst, d, q);
    input  clk, rst, d;
    output q;
    reg q;
    always @ (posedge clk) begin // posedge or negedge
        if(rst)
            q <=1'b0;
        else
            q <= d
        end
    endmodule
```

Note:

- 1: Sequential logic circuit implemented by “Always” block is edge triggered.
- 2: Describing sequential logic circuit can only use **non-blocking** assignments.

Remark: differences between blocking and non-blocking assignments

- Non-blocking Assignment
 - use “<=”.
 - Only in “Always” block
 - All assigning statements calculate their right value simultaneously, then update their left value.
- Blocking assignment
 - use “=”
 - Sequential execution in an “Always” block

```
wire a;
reg b, c;
assign a = 1'b1;
always @(posedge clk or negative reset)
    if(!reset) begin
        b <= 0;
        c <= 1;
    end
    else begin
        b <= a;
        c <= b;
    end
end
//when the first signal comes, b=0, c=1;
//when the second signal comes, b=1, c=0.
```

Non-blocking

```
wire a;
reg b, c;
always @(a or b)
    begin
        b = a;
        c = b;
    end
end
```

Suppose initial values: a=b=c=0,
when a = 1, b = c = 1.

Blocking

Blocking Assignments Collision

```
module fbosc1 (y1, y2, clk, rst);
```

```
output reg y1, y2;
```

```
input clk, rst;
```

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y1 = 0; // reset
```

```
else y1 = y2;
```

```
end
```

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y2 = 1; // preset
```

```
else y2 = y1;
```

```
end
```

```
endmodule
```

After Reset, $y1 = 0$, $y2 = 1$;

Suppose “else” statement in the first “always” block is executed first, then we get $y1 = y2 = 1$.

If “else” statement in the second “always” block is executed first, then $y1 = y2 = 0$.

Collision leads to instability.

Exercise: Nonblocking assignment

```
module fbosc1 (y1, y2, clk, rst);
```

```
output reg y1, y2;
```

```
input clk, rst;
```

After Reset, $y1 = 0$, $y2 = 1$

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y1 <= 0; // reset
```

```
else y1 <= y2;
```

```
end
```

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y2 <= 1; // preset
```

```
else y2 <= y1;
```

```
end
```

```
endmodule
```

Exercise: Nonblocking assignment

```
module fbosc1 (y1, y2, clk, rst);
```

```
output reg y1, y2;
```

```
input clk, rst;
```

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y1 <= 0; // reset
```

```
else y1 <= y2;
```

```
end
```

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if (!rst) y2 <= 1; // preset
```

```
else y2 <= y1;
```

```
end
```

```
endmodule
```

After Reset, $y1 = 0$, $y2 = 1$;

Second step: the right-hand side of “else” statement in two “always” block is executed simultaneously. Then assign values to left-hand side simultaneously. So the result is $y1 = 1$ and $y2 = 0$.

Summary:

Blocking and Non-blocking Assignment

Combinational logic circuit with “**Assign**” statement uses “=”;
Data type: **wire**.

Combinational logic circuit with “**Always**” statement uses “=”;
Data type: **reg**. (In some cases, using non-blocking assignment is also correct)

Sequential logic circuit with “**Always**” statement uses “<=”.
(Blocking assignment leads to instability)

D-Flip-flops

Flip-flops

The truth table for a positive-edge triggered D flip-flop shows an up arrow to remind you that it is sensitive to its D input only on the rising edge of the clock; otherwise it is latched. The truth table for a negative-edge triggered D flip-flop is identical except for the direction of the arrow.

Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
1	↑	1	0	SET
0	↑	0	1	RESET

(a) Positive-edge triggered

Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
1	↓	1	0	SET
0	↓	0	1	RESET

(b) Negative-edge triggered


D Flip-Flop in Verilog

Asynchronous reset:

```
module asynrst_DFF(clk, rst, d, q);
    input clk, rst, d;
    output q;
    reg q;
    always @(posedge clk or posedge rst)
        if(rst)
            q <= 1'b0;
        else
            q <= d;
endmodule
```


Synchronous reset:
 
```
module synrst_DFF(clk, rst, d, q);
    input clk, rst, d;
    output q;
    reg q;
    always @(posedge clk)
        if(rst)
            q <= 1'b0;
        else
            q <= d;
endmodule
```



D flip-flop is an information storage device with memory function and two stable states. It is the most basic logic unit of a variety of sequential circuits and an important unit circuit in digital logic circuits.

D Flip-Flop: analysis of working state

 

Analysis:

1. when clk is low level(0), T1 is open, the signal of input d is transited to \bar{q} , when clk changes from low level to high level(posedge), T3 will be open, the value of \bar{q} will be outputed.
2. when clk remains high level, T1 keeps close, whatever changes input d makes, it will not be transitted to the output.